

Reg. No.:



Name:

University of Kerala

W6713

Third Semester FYUGP Degree Examination, November 2025

Discipline Specific Core Course

PHYSICS

UK3DSCPHY200 - Basic Electronics

Academic Level: 200-299

2024 Admission

Time: 1 Hour 30 Minutes(90 Mins.)

Max. Marks: 42

Part A. 6 Marks.Time:6 Minutes.(Cognitive Level:Remember(RE)/Understand(UN)) Objective Type. 1 Mark
Each.Answer all questions


Qn No.	Question	CL	CO
1	Draw the schematic symbol of OP-Amp.	RE	4
2	State the Peak Inverse Voltage (PIV) of a diode.	RE	1
3	Construct the truth table for AND gate with 2 inputs.	UN	4
4	Explain why the emitter region of a transistor is heavily doped	UN	2
5	Explain β for a transistor.	UN	2
6	Explain operating point of an amplifier.	UN	3


Part B.8 Marks.Time:24 Minutes.(Cognitive Level:Understand(UN)/Apply(AP))Short Answer. 2 marks each.Answer all questions

Qn No.	Question	CL	CO
7	Explain the concept of Zener breakdown voltage in a Zener diode. Discuss the factors affecting the value of Zener breakdown voltage.	UN	1
8	Describe different terminals in a transistor	UN	2
9	Illustrate the need for transistor biasing.	AP	3
10	Using Boolean algebra, verify the identity: $AC + ABC = AC$	AP	4

Part C. 28 Marks.Time:60 Minutes (Cognitive Level:Apply(AP)/Analyse(AN)/Evaluate(EV)/Create(CR)) Long Answer.7 marks each.Answer all 4 Questions choosing among options * within each question

Qn No.	Question	CL	CO
11	A) Apply your understanding of transistor characteristics to set up and conduct an experiment to study the behavior of a transistor in the common-base (CB) configuration. Sketch and label the input and output characteristic curves, and analyze the relationship between input current, output current, and applied voltages. OR B)	AP	2, 2

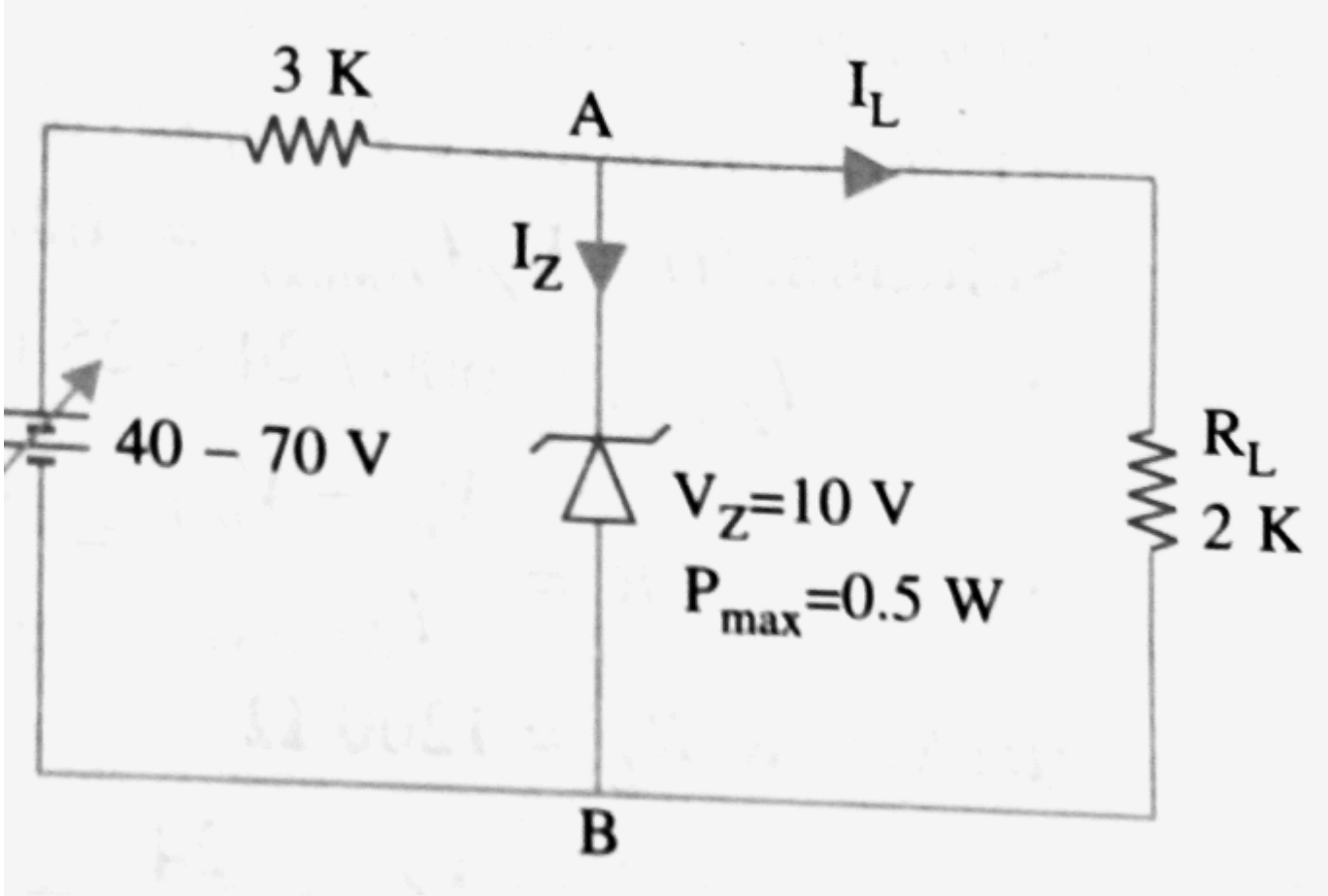Qn No.	Question	CL	CO
	Using your understanding of transistor operation, Explain the input and output characteristics of a transistor in the common-emitter (CE) configuration.		
12	<p>A)</p> <p>Discuss the importance of the series resistor in the voltage regulator circuit constructed using a Zener diode. Analyze the given circuit and calculate the battery current I.</p> 	AN	1, 1
	<p>OR</p> <p>B)</p> <p>Interpret the VI characteristics curve of a PN junction diode and explain the behavior in different biasing conditions</p>		
13	<p>A)</p> <p>The figure given below shows the DC load line and output characteristics of a transistor. By applying your understanding of transistor biasing and amplifier operation, evaluate which of the two zero-signal collector currents (Q-points) is more suitable for designing a common-emitter (CE) transistor amplifier. Justify your choice</p>	EV	3, 3

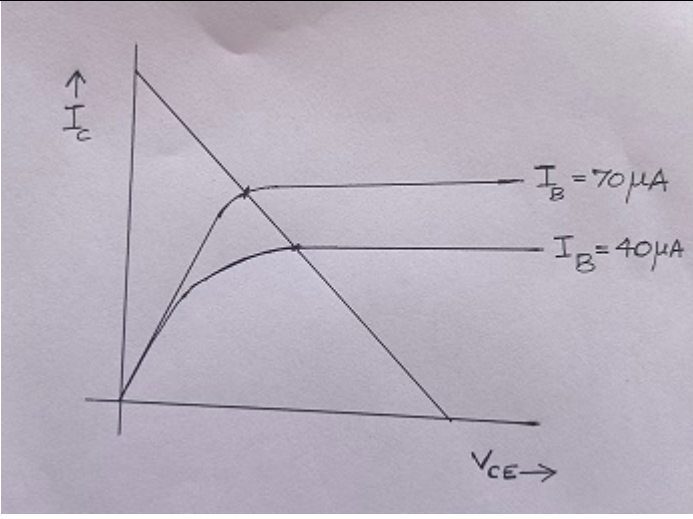Qn No.	Question	CL	CO
	 <p>OR</p> <p>B)</p> <p>A transistor uses potential divider method of biasing. $R_1 = 50k\Omega$, $R_2 = 10k\Omega$ and $R_E = 1k\Omega$. If $V_{CC} = 12V$,</p> <p>Evaluate (i) The value of I_C; given $V_{BE} = 0.1V$ (ii) The value of I_C; given $V_{BE} = 0.3V$</p>		
14	<p>A)</p> <p>Create logic circuit for Boolean Function $F=x'y'z+x'yz+xy'+xz$ and obtain its truth table. Simplify this function using boolean identities and develop the logic circuit for the same.</p> <p>OR</p> <p>B)</p> <p>Design and construct opamp inverting amplifier circuit and derive the expression for its voltage gain.</p>	CR	4, 4